

Bushra Hossain - 2031346642, Md. Ishtiaq Ahamed
Fahim - 2012518642, Tajrian Al Israq - 2021536643
LAB-1

Spring 2022
EEE/ETE 141L
Electrical Circuits-I Lab(Sec-10)
Faculty : Md. Abu Obaidah (AbO)
Instructor: Farhana Atuyar Saleh

Lab No.: 01

Date of Performance :16/02/2022	Name: 1. Bushra Hossain 2. Md. Ishtiaq Ahamed Fahim 3. Tajrian Al Israq
Date of Submission :23/02/2022	ID: 1. 2031346642 2. 2012518642 3. 2021536643

E-I

Objective:

- ① We have to find the resistance of a resistor from its color code.
- ② We have to measure voltage, current and resistance values using a digital multimeter.
- ③ We have to verify the validity of ohm's law.
- ④ We have to test the voltage divider rule in a series circuit.

Component list:

- Trainer board
- Resistors ($3.3\text{ k}\Omega$, $5.6\text{ k}\Omega$)

- Digital Multimeters (DMM)
- connecting wire
- Multimeter

Circuit diagram:

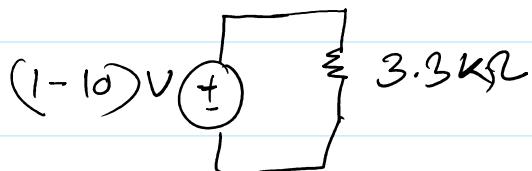


Fig : circuit : 1

Table - 1

Resistance using color	Resistance + tol	Resistance using DMM	% Error
Band 1 Band -2 Band -3 Band -4			
Orange Orange Red Gold	$3.3 \pm 5\%$	3.3 k	0%
Green Blue Red Gold	$5.6 \pm 5\%$	5.6 k	0%

Table - 2

3.3kΩ	Experimental voltage Current $I_{10^{-9}}$	Reading Voltage IR Power J_R mW
2	6	2 1.21
4	12	4 4.85
6	18	6 10.9
8	24	8 19.9
10	30	10 30.3

Table - 3

5.6 kΩ	Experimental Voltage Current $\frac{I}{10^{-3}}$	Reading Voltage IR	Power I^2R mW
2	3.5	2	0.71
4	7.1	4	2.85
6	10	6	6.43
8	14	8	11.43
10	17	10	17.86

Results : From table 2,

when, $V = 3V$, $I = 0.606 \text{ mA}$, $R = 3.3 \text{ k}\Omega$

$$\text{Power, } I^2R = (0.606)^2 \times 3.3 \text{ mW} \\ = 1.212 \text{ mW}$$

When, $V = 4V$, $I = 1.212 \text{ mA}$, $R = 3.3 \text{ k}\Omega$

$$\text{Power, } I^2 R = (1.212 \text{ mA})^2 \times 3.3 \text{ k}\Omega$$
$$= 4.818 \text{ mW}$$

$$\text{Power}_6 = I_6^2 R = (1.818)^2 \times 3.3$$
$$= 10.908 \text{ mW}$$

$$\text{Power}_8 = I_8^2 R = (2.424)^2 \times 3.3$$
$$= 19.392 \text{ mW}$$

$$\text{Power}_{10} = I_{10}^2 R = (3.030)^2 \times 3.3$$
$$= 30.3 \text{ mW}$$

For Table 3,

$$\text{Power}_2 = I_2^2 R = (0.357)^2 \times 5.6$$
$$= 0.716 \text{ mW}$$

$$\text{Power}_4 = I_4^2 R = (0.714)^2 \times 5.6$$
$$= 2.856 \text{ mW}$$

$$\text{Power}_6 = I_6^2 R = (1.071)^2 \times 5.6$$
$$= 6.426 \text{ mW}$$

$$\text{Power}_8 = I_8^2 R = (1.429)^2 \times 5.6$$
$$= 11.432 \text{ mW}$$

$$\text{Power}_{10} = I_{10}^2 R = (1.786)^2 \times 5.6$$

Current flow = 17.86 mA

Question / Answer:

1

1. State Ohm's law

State Ohm's law:

Current through a conductor between two points is directly proportional to the voltage across the two points

-

$I \propto V$

which with a constant Resistance yield

$$V = RI$$


(2)

2. Plot V vs I graph for each resistor value in same graph

Plotting V vs I graph for each resistor value in graph

As we getting Data from medium we get the value from multi-meter and plotting the value on graph

V	$I_{3.3} (10^{-4})$	$I_{5.0} (10^{-4})$
1	3	1.7
2	6	3.5
3	9	5.3
4	12	7.1
5	15	8.9
6	18	10
7	21	12
8	24	14
9	27	16
10	30	17

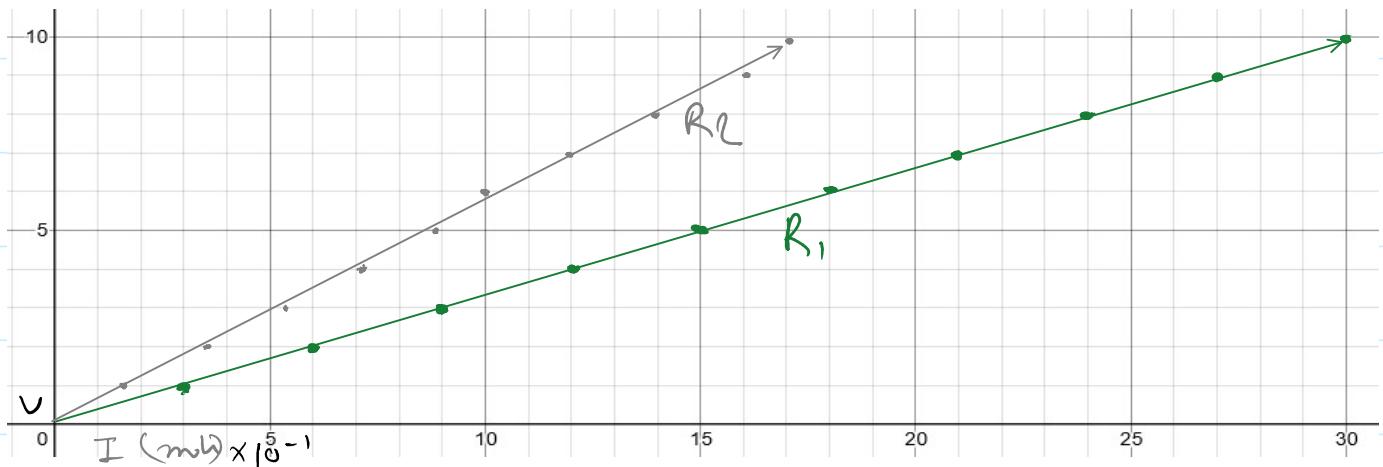

(3)

3. Does your experimental circuit follow ohm's law? Explain how you figured it out.

given variable voltage $V \{1-10\}$, while
 $R_s \{3.3\text{k}\Omega, 5.6\text{k}\Omega\}$

As we know,

$$V = IR$$

$$I = \frac{V}{R}$$

V	$I = \frac{V}{R_1} (10^9)$ $R_1 = 3.3\text{k}\Omega$	$I = \frac{V}{R_2} (10^9)$ $R_2 = 5.6\text{k}\Omega$
1	3	1.7
2	6	3.5
3	9	5.3
4	12	7.1
5	15	8.9
6	18	10

5	15	8.9
6	18	10
7	21	12
8	24	14
9	27	16
10	30	17

This graph is identical to (ex-2) making it so that multimeter form multimeter is same Ohm's law.

④

4. Calculate the resistance of each circuit using the slope of your V vs I graphs. Compare these graph values to the measured R values using DMM. Find the percentage difference.

We know that

$$\text{slope (m)} = \frac{R_{\text{ire}}}{R_{\text{un}}}$$

Here we get

$$R = \frac{V}{I}$$

from graph in multimeter

	multimeter		Ohm's law	
	R (kΩ)	R' (kΩ)	R (kΩ)	R' (kΩ)
1	3.3	5.6	3.3	5.8
2	3.3	5.6	3.3	5.8
3	3.3	5.6	3.3	5.6
4	3.3	5.6	3.3	5.6
C	3.3	5.6	3.2	5.6

4	3.3	5.6	3.3	5.6
5	3.3	5.6	3.3	5.6
6	3.3	5.6	3.3	5.6
7	3.3	5.6	3.3	5.6
8	3.3	5.6	3.3	5.6
9	3.3	5.6	3.3	5.6
10	3.3	5.6	3.3	5.6

$$\sum R = 33$$

$$\sum R' = 56$$

$$\sum R = 33$$

$$\sum R' = 56$$

multimeter mean

$$M_R = \frac{\sum R}{N} = \frac{33}{10} = 3.3$$

$$M_{R'} = \frac{\sum R'}{N} = \frac{56}{10} = 5.6$$

ohm mea. N -

$$M_{\bar{R}} = \frac{\sum \bar{R}}{N} = \frac{33}{10} = 3.3$$

$$M_{\bar{R}'} = \frac{\sum \bar{R}'}{N} = \frac{56}{10} = 5.6$$

$$\text{difference } R_{3.3} = (M_R - M_{\bar{R}}) = \frac{(3.3 - 3.3)}{10} \% \\ = 0\%$$

$$\text{difference } \bar{R}_{5.6} = (M_{R'} - M_{\bar{R}'}) = (5.6 - 5.6) \% \\ = 0\%$$

So there is no difference between
as they identical

E-2

Objective:

- Learn how to connect a series circuit on a breadboard
- Validate the voltage divider rules
- Verify Kirchhoff's voltage law

Component list:

- Trainer board
- Resistors ($3.3\text{ k}\Omega$, $4.7\text{ k}\Omega$, $5.6\text{ k}\Omega$)
- Digital Multimeter (DMM)
- Connecting wire

Circuit Diagram:

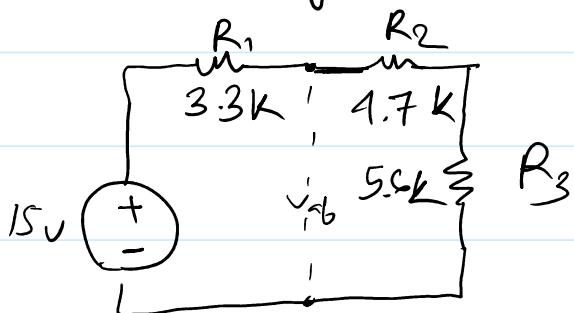


Fig: circuit

Table-1

Resistance using colour coding				Resistance of DMM	%Error
Band-1	Band-2	Band-3	Band-4	Resistance tol	
Orange	Orange	Red	Gold	$3.3 \pm 5\%$	3.3
Yellow	Violet	Red	Gold	$4.7 \pm 5\%$	4.7
Green	Blue	Red	Gold	$5.6 \pm 5\%$	5.6

Table-2

Experimental reading					Theoretical values				
V_s	V_{R_1}	V_{R_2}	V_{R_3}	V_s	V_{R_1}	V_{R_2}	V_{R_3}	V_s	
15	3.690	5.189	6.176	3.690				5.189	6.176
% Error									
V_s		V_{R_1}			V_{R_2}		R_3		
15		0			0.0779.		0.0659.		

Table-3

Potential rise	Potential drop ($V_{R_1} + V_{R_2} + V_{R_3}$)	Are voltage & current equal Yes
15 V	$(3.69 + 5.189 + 6.176) = 15 V$	

Table-4

Experimental reading		Theoretical values	
V_{ab}	R_{eq}	V_{ab}	R_{eq}
11.36 V	13.6 Ω	11.36 V	13.6 Ω
	0%	Error	
V_{ab}		R_{eq}	
09.		09.	

Results: We know, $V_X = \frac{E \times R_X}{R_T}$

$$R_T = R_1 + R_2 + R_3 = 3.3 + 4.7 + 5.6 \text{ k}\Omega \\ = 13.6 \text{ k}\Omega$$

$$V_{R_1} = \frac{3.3 \times 15}{13.6} = 3.64 \text{ k}\Omega$$

$$V_{R_2} = \frac{4.7 \times 15}{13.6} = 5.18 \text{ k}\Omega$$

$$V_{R_3} = \frac{5.6 \times 15}{13.6} = 6.18 \text{ k}\Omega$$

$$\% \text{ Error} = \frac{\text{Theoretical value} - \text{Experiment value}}{\text{Theoretical value}} \times 100\%$$

$$\text{For } V_S, \% \text{ Error} = \frac{15 - 15}{15} \times 100\% \\ = 0\%$$

$$\text{For } V_{R_1}, \% \text{ Error} = \frac{3.64 - 3.64}{3.64} \times 100\% \\ = 0\%$$

$$\text{For } V_{R_2}, \% \text{ Error} = \frac{5.184 - 5.18}{5.184} \times 100\% \\ = 0.077\%$$

$$\text{For } V_{R_3}, \% \text{ Error} = \frac{6.18 - 6.176}{6.18} \times 100\% \\ = 0.065\%$$

$$V_{ab} = 5.18 + 6.18 = 11.36 \text{ V}$$

$$R_{eq} = 3.3 \text{ k}\Omega + 4.7 \text{ k}\Omega + 5.6 \text{ k}\Omega \\ = 13.6 \text{ k}\Omega$$

Question / Answer :

1

1. State the voltage division rule.

Voltage division Rule:

When in a series circuit is connected the current remain the same but voltage is devideed by by the multitude of each resistor

$$V_x = \frac{E}{R_T} R_x$$

Diagram illustrating the formula:

- V_x → Voltage of X Resistor
- E → Voltage of circuit
- R_x → magnitude of X Resistor
- R_T → Total Resistor of circuit

2

2. State the Kirchhoff's voltage law (KVL)

Kirchhoff's voltage law (KVL) states that the voltage around a closed path algebraically sum to zero. In other words, the sum of voltage rise equals the sum of voltage drop.

The equation is,

$$\sum_{M=0}^m V_m = 0$$

(3)

3. Showing all steps, calculate the theoretical values in Table 2. Compare theoretical values to your experimental values and explain whether your circuit follows KVL or not

Table-2

Experimental reading:

$$\begin{aligned}
 R_s \text{ (total resistance)} &= R_1 + R_2 + R_3 \\
 &= 3.3 + 4.7 + 5.6
 \end{aligned}$$

$$= 13.8 \Omega$$

$$V_s = I_s R_s \\ I_s = \frac{V_s}{R_s} = \frac{15}{13.6} = 1.103 A$$

$$V_{R_1} = I_s R_1 = 3.640 V$$

$$V_{R_2} = I_s R_2 = 5.189 V$$

$$V_{R_3} = I_s R_3 = 6.176 V$$

Theoretical values:

$$R'_{\text{S}} (\text{total Resistance}) = R_1 + R_2 + R_3 \\ = 3.3 + 4.7 + 5.6 \\ = 13.6 \Omega$$

$$V'_s = I_s R'_s$$

$$I'_s = \frac{V'_s}{R'_s} = \frac{15}{13.6} = 1.103 A$$

$$V'_{R_1} = I_s R_1 = 3.640 V$$

$$V'_{R_2} = I_s R_2 = 5.189 V$$

$$V'_{R_3} = I_s R_3 = 6.176 V$$

Error:

$$\% \text{ Error} = \frac{(V_s - V'_s)}{V_s} \times 100\% = \frac{(15 - 15)}{15} \times 100\% \\ \approx 0\%$$

$$v_1 = \frac{(v_1 - v_1')}{v_1} \times 100\% = \frac{3.69 - 3.69}{v_1} \times 100\%, \\ \approx 0\%.$$

$$v_2 = \left(\frac{v_2 - v_2'}{v_1} \right) 100\% = \frac{5.184 - 5.18}{2} \times 100\%, \\ \approx 0.077\%$$

$$v_3 = \left(\frac{v_3 - v_3'}{v_3} \right) 100\% = \frac{0}{v_3} \times 100\%, \\ \approx 0.065\%$$

So, voltage Rise $\approx 15\text{V}$

voltage drop $= v_1 + v_2 + v_3 = 15\text{V}$

voltage Rise $=$ voltage drop

which follows KVL

④

4. Showing all the calculations, theoretically calculate V_{ab} . Compare with the experimental value and verify the voltage division rule at the terminal a-b.

Theoretical calculation:

$$\begin{aligned}
 V_{ab} &= V - V_a \\
 &= 15 - I_s R_s \\
 &= 15 - 3.69 = 13.36 \text{ V}
 \end{aligned}$$

To measure Theoretical voltage
we use multimeter place between ab
and by measuring voltage we get

$$V'_{ab} = 13.36 \text{ V}$$

Error:

$$\begin{aligned}
 \text{Error} &= \frac{\text{Theoretical} - \text{Experiment}}{\text{Theoretical}} \times 100\% \\
 &= \frac{V_{ab} - V'_{ab}}{V_{ab}} \times 100\% = 0\%
 \end{aligned}$$

As the result is almost same we can
say that voltage division rule at
the terminal a-b is verified.

(S)

5. Showing all the steps, calculate R_{eq} . Compare with the experimental value.

R_{eq} by Theoretical value:

$$R_{eq} = R_1 + R_2 + R_3 = 3.3 + 4.7 + 5.6 = 13.6 \Omega$$

R_{eq} by Experimental value:

R'_{eq} by measuring via multimeter we get

$$R'_{eq} = R'_1 + R'_2 + R'_3 = 3.3 + 4.7 + 5.6 = 13.6 \Omega$$

So, theoretical and experimental value for are same.

Discussion:

From the lab 1. we learned about ohm's law, Kirchhoff's voltage law and voltage divider rule using series circuit.

As, it was an online lab, we had to use multimeter to do the experiment.

So, we didn't have to face many errors

Both matlism and Ohms law had same result as it doesn't have flaws which is present in real world which could be coming from tolerance equipment in accuracy and also form loss connection. But it help creating proof and validation of ohms law.