

# North South University

## ECE

### Lab Report - 1

Experiment No: 1&2

Experiment Title: Verification of Ohm's Law & Series Circuit

Course Code: EEE141L

Course Name: Electrical Circuit Lab

Name & ID: Md. Ishtiaq Ahamed Fahim 2012518642

Date of Experiment: 23.2.2022

Date of Submission: 23.2.2022

E-1

Objective: The objective is to verify Ohm's

law using both math and a Multimeter.  
keeping in mind how to verify and  
measure resistance.

Component list:

- Trainer board
- Resistor (3.3 k $\Omega$ , 5.6 k $\Omega$ )
- Digital Multimeter (DMM)
- connecting wire
- Multimeter

Circuit diagram:



Fig: circuit : 1

Table - 1

Resistance using color		using	color	Resistance $\pm$ tol	Resistance using DMM	% Error
Band-1	Band-2	Band-3	Band-4			
Orange	Orange	Red	Gold	$33 \pm 5\%$	3.3 k	0%
Green	Blue	Red	Gold	$5.6 \pm 5\%$	5.6 k	0%

Table - 2

3.3k $\Omega$	Experimental		Reading
voltage	Current $I$ $10^{-4}$	voltage $IR$	Power $I^2R$ mW
2	6	2	1.21
4	12	4	4.85
6	18	6	10.9
8	2.4	8	19.4
10	3	10	30.303

Table - 3

5.6k $\Omega$	Experimental		Reading
voltage	Current $I$ $10^{-4}$	voltage $IR$	Power $I^2R$ mW
2	3.5	2	0.71
4	7.1	4	2.85
6	10	6	6.43
8	14	8	11.43
10	1.7	10	17.86

Question / Answer:

①

State Ohm's law:

Current through a conductor between two points is directly proportional to the voltage across the two points

$$I \propto V$$

which with a constant Resistance yields

$$V = RI$$


②

Plotting  $V$  vs  $I$  graph for each resistor value in graph

As we getting Data from multimeter we get the value from multi-meter and plotting the value on graph

$V$	$I_{3.3} (10^{-4})$	$I_{5.6} (10^{-4})$
1	3	1.7
2	6	3.5
3	9	5.3
4	12	7.1
5	15	8.9
6	18	10
7	21	12
...	...	...

6	18	10
7	21	12
8	24	14
9	27	16
10	30	17

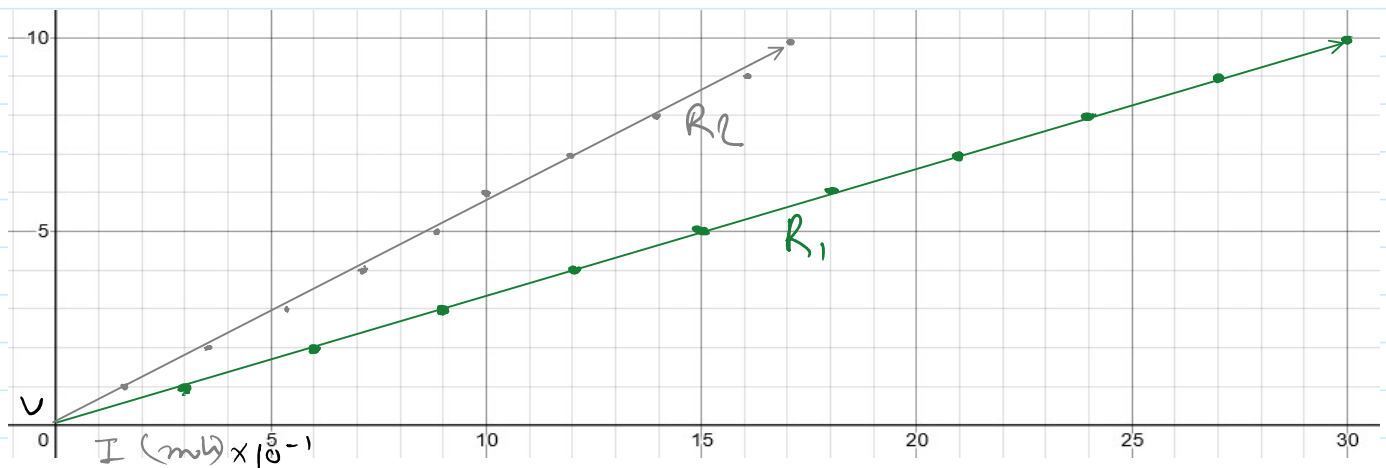

3

given variable voltage  $V \{1-10\}$ , while  
 $R = \{3.3k\Omega, 5.6k\Omega\}$

As we know,

$$V = IR$$

$$I = \frac{V}{R}$$

$V$	$I = \frac{V}{R_1} (10^{-9})$ $R_1 = 3.3k\Omega$	$I = \frac{V}{R_2} (10^{-9})$ $R_2 = 5.6k\Omega$
1	3	1.7
2	6	3.5
3	9	5.3
4	12	7.1

3	9	5.3
4	12	7.1
5	15	8.9
6	18	10
7	21	12
8	24	14
9	27	16
10	30	17

This graph is identical to (ex-2) making it so that multimeter forms multimeter in same Ohm's law.

④

we know that

$$\text{slope (m)} = \frac{R_{\text{me}}}{R_{\text{un}}}$$

Here we get

$$R = \frac{V}{I}$$

form graph in multimeter

	multimeter		ohm's law	
	R (k $\Omega$ )	R' (k $\Omega$ )	R (k $\Omega$ )	R' (k $\Omega$ )
1	3.3	5.6	3.3	5.6
2	3.3	5.6	3.3	5.6
3	3.3	5.6	3.3	5.6
4	3.3	5.6	3.3	5.6
5	3.3	5.6	3.3	5.6
6	3.3	5.6	3.3	5.6
7	3.3	5.6	3.3	5.6

7	3.3	5.6	3.3	5.6
7	3.3	5.6	3.3	5.6
8	3.3	5.6	3.3	5.6
9	3.3	5.6	3.3	5.6
10	3.3	5.6	3.3	5.6

$$\sum R = 33$$

$$\sum R' = 56$$

$$\sum R = 3.3$$

$$\sum R' = 5.6$$

multimeter mean

$$M_R = \frac{\sum R}{N} = \frac{33}{10} = 3.3$$

$$M_{R'} = \frac{\sum R'}{N} = \frac{56}{10} = 5.6$$

ohm mean:  $N$

$$M_{\bar{R}} = \frac{\sum \bar{R}}{N} = \frac{33}{10} = 3.3$$

$$M_{\bar{R}'} = \frac{\sum \bar{R}'}{N} = \frac{56}{10} = 5.6$$

$$\text{difference } R_{3.3} = (M_R - M_{\bar{R}}) = \frac{(3.3 - 3.3)}{10} \% = 0\%$$

$$\text{difference } \bar{R}_{5.6} = (M_{R'} - M_{\bar{R}'}) = \frac{(5.6 - 5.6)}{10} \% = 0\%$$

So there is no difference between  
as they identical

Discussion:

Both multisim and Ohm's law had same result as it doesn't have flaws which is present in real world which could be coming from tolerance equipment in accuracy and also from loose connection. But it helps in erecting proof and validation of Ohm's law.

## E-2

Objective:

- learn how to connect a series circuit on a breadboard



- validate the voltage divider rules
- verify Kirchhoff's voltage law

Component list:

- Trainer board
- Resistors ( $3.3k\Omega$ ,  $4.7k\Omega$ ,  $5.6k\Omega$ )
- Digital Multimeter (DMM)
- Connecting wire

Circuit Diagram:

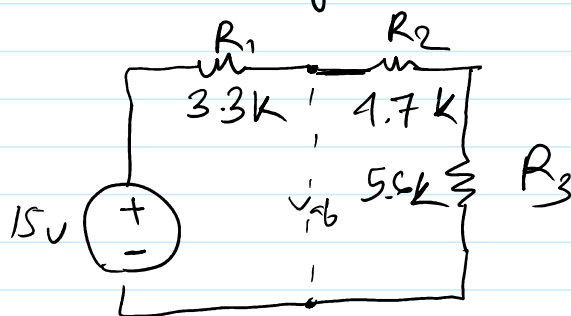


Fig: circuit

Table-1

Resistance using colour coding					Resistance of DMM	% Error
Band-1	Band-2	Band-3	Band-4	Resistance $\pm$ tol		
Orange	Orange	Red	Gold	$3.3 \pm 5\%$	3.3	0
Yellow	Violet	Red	Gold	$4.7 \pm 5\%$	4.7	0
Green	Blue	Red	Gold	$5.6 \pm 5\%$	5.6	0

Table-2

Experimental readings				Theoretical values			
$V_S$	$V_{R_1}$	$V_{R_2}$	$V_{R_3}$	$V_S$	$V_{R_1}$	$V_{R_2}$	$V_{R_3}$
15	3.640	5.184	6.176	3.640		5.184	6.176
% Error							
$V_S$		$V_{R_1}$		$V_{R_2}$		$V_{R_3}$	
15		0		0		0	

Table-3

Potential rise 15 V	Potential drop ( $V_{R_1} + V_{R_2} + V_{R_3}$ ) (3.64 + 5.184 + 6.176) = 15 V	Are voltage rises and drops equal and Yes
------------------------	---	--

Table-4

Experimental readings		Theoretical values	
$V_{ab}$	$R_{eq}$	$V_{ab}$	$R_{eq}$
11.36 V	13.6 $\Omega$	11.36 V	13.6 $\Omega$
	% Error		
$V_{ab}$		$R_{eq}$	
0		0	

Question/Answer:

①

Voltage division Rule:

When in a series circuit is connected

the current remain the same but voltage is divided by by the multitude of each resistor

$$V_x = \frac{E R_x}{R_T}$$

voltage of circuit →  $E$   
 magnitude of  $x$  Resistor →  $R_x$   
 voltage of  $x$  Resistor →  $V_x$   
 Total Resistor of circuit →  $R_T$

2

Table-2

Experimental reading:

$$\begin{aligned}
 R_S \text{ (total Resistance)} &= R_1 + R_2 + R_3 \\
 &= 3.3 + 4.7 + 5.6 \\
 &= 13.6 \Omega
 \end{aligned}$$

$$\begin{aligned}
 V_S &= I_S R_S \\
 I_S &= \frac{V}{R_S} = \frac{15}{13.6} = 1.103 \text{ A}
 \end{aligned}$$

$$V_{R_1} = I_S R_1 = 3.640 \text{ V}$$

$$V_{R_2} = I_S R_2 = 5.184 \text{ V}$$

$$V_{R_3} = I_S R_3 = 6.176 \text{ V}$$

theoretical values:

$$\begin{aligned} R'_S \text{ (total Resistance)} &= R_1 + R_2 + R_3 \\ &= 3.3 + 4.7 + 5.6 \\ &= 13.6 \Omega \end{aligned}$$

$$V'_S = I'_S R'_S$$

$$I'_S = \frac{V'_S}{R'_S} = \frac{15}{13.6} = 1.103 \text{ A}$$

$$V'_{R_1} = I'_S R_1 = 3.640 \text{ V}$$

$$V'_{R_2} = I'_S R_2 = 5.189 \text{ V}$$

$$V'_{R_3} = I'_S R_3 = 6.176 \text{ V}$$

Error:

$$\begin{aligned} V_S &= \frac{(V_S - V'_S)}{V_S} \times 100\% = \frac{0}{V_S} \times 100\% \\ &= 0\% \end{aligned}$$

$$\begin{aligned} V_1 &= \frac{(V_1 - V'_1)}{V_1} \times 100\% = \frac{0}{V_1} \times 100\% \\ &= 0\% \end{aligned}$$

$$\begin{aligned} V_2 &= \left( \frac{V_2 - V'_2}{V_2} \right) 100\% = \frac{0}{V_2} \times 100\% \\ &= 0\% \end{aligned}$$

$$\begin{aligned} V_3 &= \left( \frac{V_3 - V'_3}{V_3} \right) 100\% = \frac{0}{V_3} \times 100\% \\ &= 0\% \end{aligned}$$

4

Theoretical calculation:

$$\begin{aligned}V_{ab} &= V - V_a \\&= 15 - I R_s \\&= 15 - 3.69 = 13.36 \text{ V}\end{aligned}$$

To measure Theoretical value  
we use multimeter place between a b  
and by measuring voltage we get

$$V_{ab} = 13.36 \text{ V}$$

Error:

$$\text{Error} = \frac{\text{Theoretical} - \text{Experiment}}{\text{Theoretical}} \times 100\%$$

$$= \frac{V_{ab} - V_{ab}}{V_{ab}} \times 100\% = 0\%$$

5

$R_{eq}$  by Theoretical value:

$$R_{eq} = R_1 + R_2 + R_3 = 3.3 + 4.7 + 5.6 = 13.6 \Omega$$

$R_{eq}$  by Experimental value:

$R'_{eq}$  by measuring via multimeter we get

$$R'_{eq} = R'_1 + R'_2 + R'_3 = 3.3 + 4.7 + 5.6 = 13.6 \Omega$$

Discussion: