

Bushra Hossain - 2031346642, Md. Ishtiaq Ahmed
Fahim - 2012518642, Tajrian Al Israq - 2021536643
LAB-2

Monday, 28 February 2022 11:00 PM

Spring 2022
EEE/ETE 141L
Electrical Circuits-I Lab(Sec-10)
Faculty : Md. Abu Obaidah (AbO)
Instructor: Farhana Atuyar Saleh

Lab No.: 02

Date of Performance :23/02/2022	Name: 1. Bushra Hossain 2. Md. Ishtiaq Ahmed Fahim 3. Tajrian Al Israq
Date of Submission :2/01/2022	ID: 1. 2031346642 2. 2012518642 3. 2021536643

Lab 2 : KCL, Current Divider Rule with Parallel and Ladder Circuit.


Objectives :


- ① We have to learn how to connect a parallel circuit on a breadboard
- ② We have to validate the current divider rules.
- ③ We have to verify Kirchhoff's current law.
- ④ We have to verify KCL and KVL in ladder circuit.

List of Components :

- ① Trainer board.
- ② Resistors [1k Ω , 3.3k Ω , 4.7k Ω , 5.6k Ω , 10k Ω)
- ③ Digital Multimeter (DMM)
- ④ Connecting wire.
- ⑤ Multisim

Circuit Diagram:

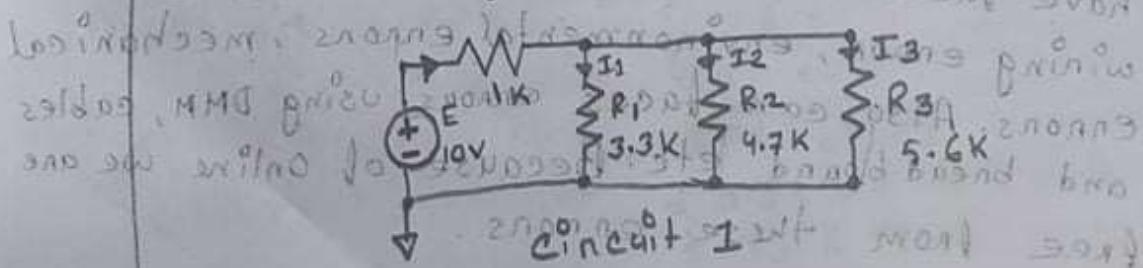

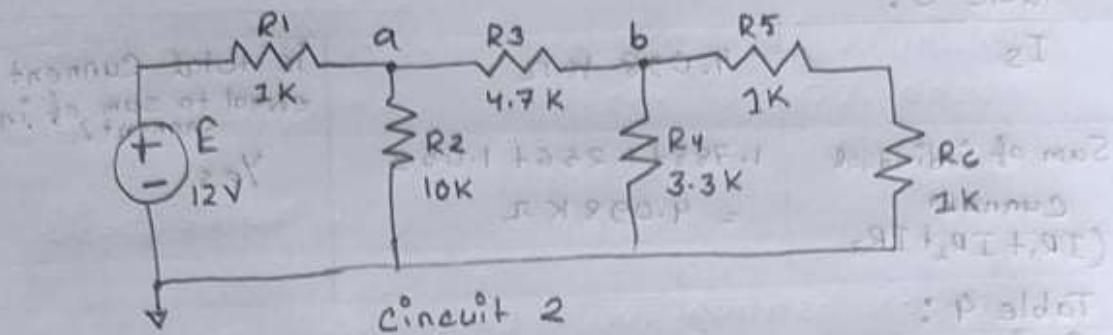

Circuit 2

Data Table:

Table 1:

Resistance using colour coding				Resistance using DMM	% Error
Band 1	Band 2	Band 3	Band 4	Resistance \pm tol	
Brown	Black	Red	Gold	$1\text{k}\Omega \pm 5\%$	$1\text{k}\Omega$ 0%
Orange	Orange	Red	Gold	$3.3\text{k}\Omega \pm 5\%$	$3.3\text{k}\Omega$ 0%
Yellow	Violet	Red	Gold	$4.7\text{k}\Omega \pm 5\%$	$4.7\text{k}\Omega$ 0%
Green	Blue	Red	Gold	$5.6\text{k}\Omega \pm 5\%$	$5.6\text{k}\Omega$ 0%
Brown	Black	Orange	Gold	$10\text{k}\Omega \pm 5\%$	$10\text{k}\Omega$ 0%


Table 2:

Experimental readings				Theoretical values			
I_s (mA)	IR_1 (mA)	IR_2 (mA)	IR_3 (mA)	I_s (mA)	IR_1 (mA)	IR_2 (mA)	IR_3 (mA)
4.098	1.788	1.256	1.054	4.1	1.8	1.26	1.054

% Error

I_s	IR_1	IR_2	IR_3
0.0498% on 0.05%	0.67%	0.317%	0%

Result:

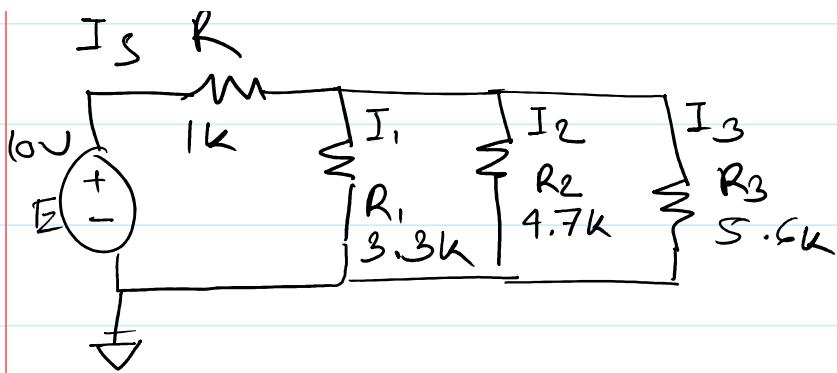

$$R_{eq} = 1k + (R_1 \parallel R_2 \parallel R_3)$$

$$= 1 + \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$

$$= 1 + \left(\frac{1}{3.3} + \frac{1}{4.7} + \frac{1}{5.6} \right)^{-1}$$


$$= 1 + 1.4$$

$$= 2.4 \Omega$$

$$E = I_T R_{eq}$$

$$10 = I_T R_{eq}$$
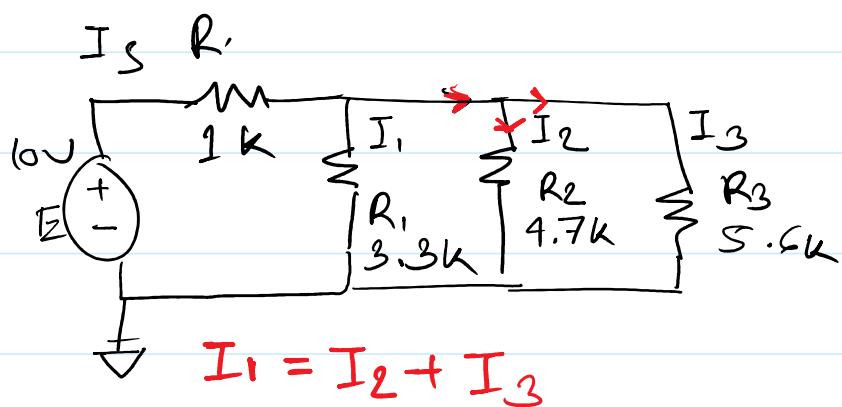
$$I_T = \frac{10}{2.4} = 4.1 \text{ mA}$$



$$I_1 = \frac{R_1 || R_2 || R_3}{R_1} I_T$$

$$\approx 1.8$$

$$I_2 = \frac{R_1 || R_2 || R_3}{R_2} I_T$$

$$\approx 1.26$$

$$I_3 = \frac{R_1 || R_2 || R_3}{R_3} I_T$$

$$\approx 1.054$$

$$I_S = \% \text{ error} = \left| \frac{4.1 - 4.098}{4.1} \right| \times 100\%$$

--

$$= 0.05\%$$

$$I_1 = \% \text{ error} = \left| \frac{1.8 - 1.788}{1.8} \right| \times 100\%.$$

$$= 0.67\%$$

$$I_2 = \% \text{ error} = \left| \frac{1.26 - 1.256}{1.26} \right| \times 100\%.$$

$$= 0.314\%$$

$$I_3 = \% \text{ error} = \left| \frac{1.059 - 1.054}{1.059} \right| \times 100$$

$$= 0.7\%$$

Table 3 :

I_s	4.098 kΩ	is total current equal to sum of individual currents?
Sum of individual currents $(I_{R1} + I_{R2} + I_{R3})$	$1.788 + 1.256 + 1.053 = 4.098 \text{ k}\Omega$	Yes

Table 4 :

Experimental Res	Theoretical Res	% Error
2.44 kΩ	2.44 kΩ	0%

Table 5 :

Component	Voltage (V)	Current (mA)
E	12	2.538
R ₁	2.53	2.538
R ₂	9.46	0.946
R ₃	7.48	1.592
R ₄	1.98	0.601
R ₅	0.99	0.991
$\sum R$ (Amm)	0.99	0.991

Table 3 Result :

$$\begin{aligned}\text{Sum of individual current} &= (1.788 + 1.256 + 1.659) \\ &= 4.098\end{aligned}$$

Table 4 Result:

$$\begin{aligned}R_{eq} &= \frac{1}{k} + (R_1 \parallel R_2 \parallel R_3) \\ &= \frac{1}{1 + \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}} \\ &= \frac{1}{1 + \left(\frac{1}{3.3} + \frac{1}{4.7} + \frac{1}{5.6} \right)^{-1}} \\ &\approx 1 + 1.49 \\ &\approx 2.49\Omega\end{aligned}$$

Table 5 Result:

$$I_1 = I_2 + I_3$$

$$I_3 = I_4 + I_5$$

we get

$$I_1 = I_2 + I_4 + I_5$$

$$V_1 = \frac{R_1}{R_{eq}} \times 12 = 2.538 \text{ V}$$

$$I_1 = \frac{V_1}{R_1} = \frac{2.538}{1} = 2.538 \text{ A}$$

$$V_2 = E - V_1 \quad [\text{voltage rule}]$$

$$= 12 - 2.538 \approx 9.46 \text{ V}$$

$$I_2 = \frac{V_2}{R_2} = \frac{9.46}{10} = 0.946 \text{ A}$$

$$V_3 = \frac{R_3}{((R_5 + R_6) \parallel R_7) + R_3} \times V_2$$

$$= \frac{4.7}{\left((1+1)^{-1} + 3 \cdot 3^{-1} \right)^{-1} + 4.7} \times 9.46$$

$$= 7.478 \text{ V}$$

$$I_3 = \frac{V_3}{R_3} = \frac{7.478}{4.7} = 1.592 \text{ A}$$

$$V_q = 9.46 - 7.478 = 1.982 \text{ V} \quad [\text{voltage rule}]$$

$$I_4 = \frac{V_q}{r} = \frac{1.982}{0.001} = 1982 \text{ A}$$

$$R_7^2 = \frac{3.3}{3.3} = 1$$

$$\begin{aligned}V_5 &= \frac{R_5}{R_5 + R_6} \times V_9 \\&= \frac{1}{1+1} \times 1.982 \\&= 0.991\end{aligned}$$

$$I_5 = \frac{V_5}{R_5} = \frac{0.991}{1} = 0.991 \text{ A}$$

$$V_6 = V_5 - V_4 = 1.982 - 0.991 = 0.991 \text{ V}$$

$$I_6 = \frac{R_6}{R_5 + R_6} \times V_4$$

$$I_6 = \frac{1}{1+1} \times 1.982 = 0.991 \text{ A}$$



Question / Answer :

① State the current division rule.

Ans: Current division rule states that the entire current separated into either of the parallel combination of two resistance or impedance is conversely corresponding to the esteem of resistance. It tells us how the current is isolated within the parallel associated resistance.

② State the Kirchhoff's current law (KCL).

Ans: Kirchhoff's current law states that "the algebraic sum of the currents entering and leaving a node is equal to zero". This law is utilized to depict how a charge enters and takes off a wire junction point on node on a wire.

(3)

③ With the experimental data, verify Kirchhoff's voltage Law in circuit 1 within each independent closed loop of the circuit.

Ans: We have to use Kirchhoff's voltage law in circuit 1 within each independent closed loop of the circuit.

$$\text{Given, } V = 10 \text{ V}$$

Now,

$$\frac{10 - V_x}{1 \text{ k}\Omega} = \frac{V_x}{3.3 \text{ k}\Omega} + \frac{V_x}{4.7 \text{ k}\Omega} + \frac{V_x}{5.6 \text{ k}\Omega}$$

$$\Rightarrow 10 - V_x = V_x \left(\frac{1}{3.3} + \frac{1}{4.7} + \frac{1}{5.6} \right) \text{ k}\Omega^{-1}$$

$$\Rightarrow 10 \text{ V} = V_x + (0.694) V_x$$

$$\Rightarrow 10 \text{ V} = V_x (1 + 0.694)$$

$$\Rightarrow 10 \text{ V} = 1.694$$

$$\Rightarrow V_x = \frac{10 \text{ V}}{1.694}$$

$$\therefore V_x = 5.901 \text{ V}$$

$$\therefore V_x = 5.901 \text{ V}$$

$$\text{Now, } I_s = \frac{(10 - 5.901) \text{ V}}{1 \text{ k}\Omega}$$

in program

$$= 4.098 \text{ mA}$$

$$\text{Now, Again } IR_1 = \frac{V_x}{R_1}$$

$$= \frac{5.901 \text{ V}}{3.3 \text{ k}\Omega}$$

$$= 1.788 \text{ mA}$$

$$IR_2 = \frac{V_x}{R_2} = \frac{5.901 \text{ V}}{4.7 \text{ k}\Omega}$$

$$= 1.256 \text{ mA}$$

$$IR_3 = \frac{V_x}{R_3} = \frac{5.901 \text{ V}}{5.6 \text{ k}\Omega}$$

$$= 1.053 \text{ mA}$$

So the experimental values are same
as the Kirchhoff's voltage law

$$I_s = IR_1 + IR_2 + IR_3$$
$$= (1.788 + 1.256 + 1.053) \text{ mA}$$

$$\therefore I_s = 4.098 \text{ mA}$$

It proves the Kinchhoff's Law.

Am 388 F. A.

Am 388 F. P.

$$\frac{V}{R} = 1.9T \quad (\text{left loop})$$

$$\frac{V - 100.6}{R + 4.4} =$$

Am 388 F. A.

$$\frac{V - 100.6}{R + 4.4} = \frac{V}{R} = 1.9T$$

Am 388 F. P.

$$\frac{V - 100.6}{R + 4.4} = \frac{V}{R} = 1.9T$$

Am 388 mA

Now calculate voltages due to source
currents and voltage drops due to

$$T_s + R_s + T_R = 2T$$

$$\text{Am} (270.1 + 24.4 + 388.1) =$$


7

With the experimental data, verify Kirchhoff's current law at nodes a and b of circuit 2.

We know Kirchoff current law states that the summation of all current entering and leaving a junction is equal to zero

$$\sum_{k=1}^n i_k = 0$$

at point ab

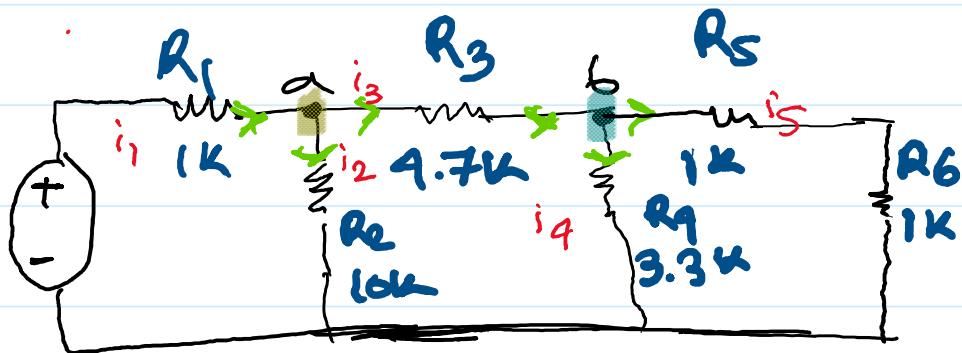

$$2.538 \text{ mA} \rightarrow \text{at } a \quad i_3 = 1.592 \text{ mA}$$

$$i_1 \quad i_2 = 0.601 \text{ mA}$$

As Kirchhoff's current law states we can derive this formula from it,

$$\sum_{\text{in}}^n \text{Current in} = \sum_{\text{out}}^n \text{Current out}$$

at Point a,

$$I_{\text{in}} = I_{\text{out}}$$

$$i_1 = i_2 + i_3$$

$$2.538 \text{ mA} = (1.592 + 0.601) \text{ mA}$$

$\leftarrow \rightarrow 0 \text{ mV}$

$$2.538 \text{ mV} = 2.538 \text{ mV}$$

proven

Alternatively:


$$\sum_{k=1}^n i_k = 0$$

$$\sum_{k=1}^n I_{in} + \sum_{k=1}^n I_{out} = 0$$

$$2.538 - 2.538 = 0$$

$$0 = 0$$

Proven

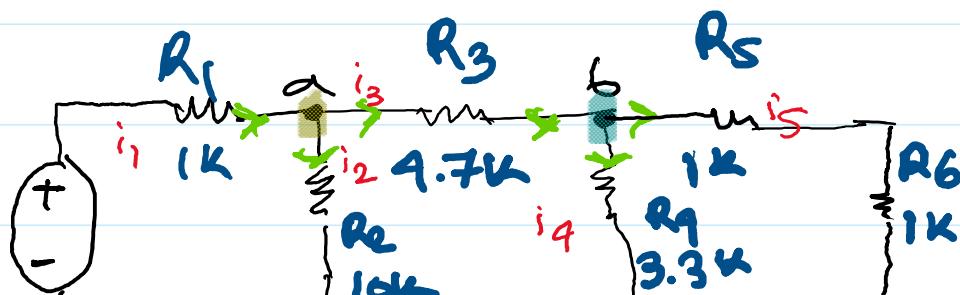




$$\text{at } b \quad i_3 = 1.592 \text{ mA}$$

$$i_Q = 0.601 \text{ mA}$$

$$i_S = 0.991 \text{ mA}$$

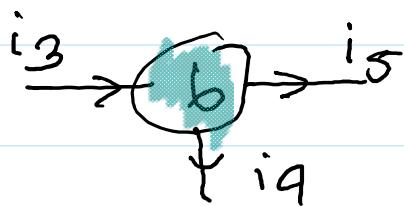

at b point

$$I_{in} = I_{out}$$

$$i_3 = i_Q + i_S$$

$$1.592 = 0.601 + 0.991$$

$$1.592 = 1.592$$

Proven

Alternatively,

$$\sum_{k=1}^n i_k = 0$$

$$I_{in} + I_{out} = 0$$


$$1.592 - 1.592 = 0$$

$$0 = 0$$

proven

(S)

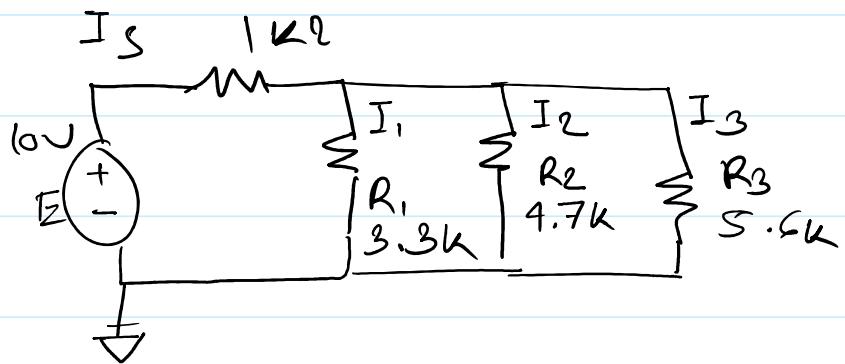Showing all steps, calculate the theoretical values in Table 2. Compare theoretical values to your experimental values and explain whether your circuit follows KCL or not




$$\begin{aligned}
 R_{eq} &= 1k + (R_1 \parallel R_2 \parallel R_3) \\
 &= 1 + \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} \\
 &= 1 + \left(\frac{1}{3.3} + \frac{1}{4.7} + \frac{1}{5.6} \right)^{-1} \\
 &= 1 + 1.44 = 2.44 \\
 &\approx 2.4 \text{ k}
 \end{aligned}$$

$$E = I_T R_{eq}$$

$$10 = I_T R_{eq}$$
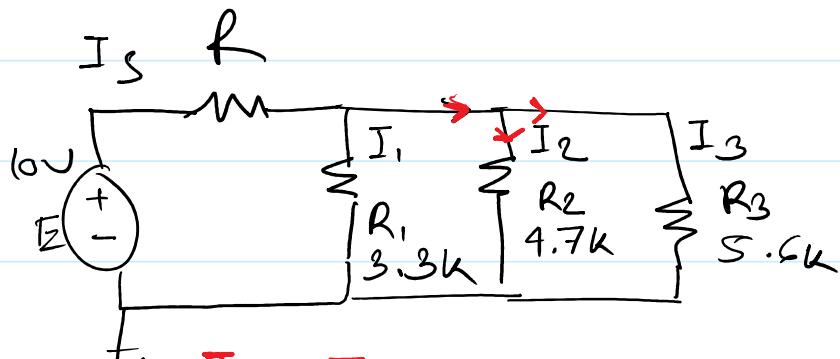
$$I_T = \frac{10}{2.4} = 4.1 \text{ mA}$$



$$I_1 = I_2 + I_3$$

$$I_1 = \frac{R_1 || R_2 || R_3}{R_1} I_T$$

$$\approx 1.74$$

$$I_2 = \frac{R_1 || R_2 || R_3}{R_2} I_T$$

$$\approx 1.22$$

$$I_3 = \frac{R_1 || R_2 || R_3}{R_3} I_T$$

$$\approx 1.03$$


$$I_S = \% \text{ error} = \left| \frac{4.1 - 4.098}{4.1} \right| \times 100\% \\ \approx 0.05\%$$


Table 2:

Experimental readings				Theoretical values			
I_S	I_{R1}	I_{R2}	I_{R3}	I_S	I_{R1}	I_{R2}	I_{R3}
1.098 mA	1.788 mA	1.256 mA	1.059 mA	4.1 mA	1.74 mA	1.22 mA	1.03 mA
% Error							
I_S		I_{R1}		I_{R2}		I_{R3}	
0.05		0.016		0.016		0.017	

Table 4:

Experimental Req	Theoretical Req	% Error
2.49 k	2.44 k	0

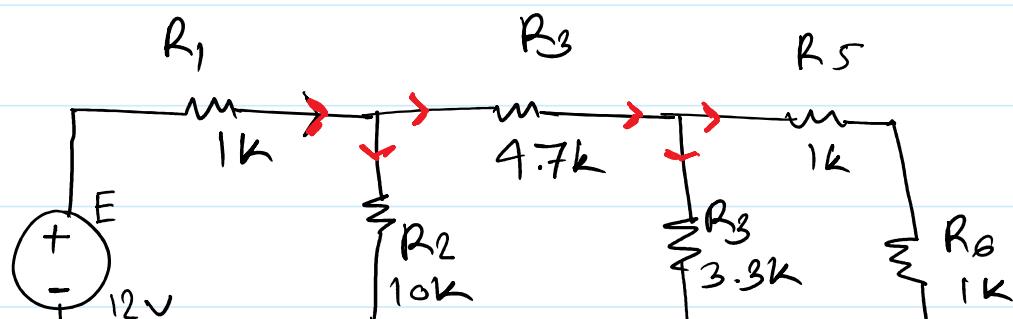

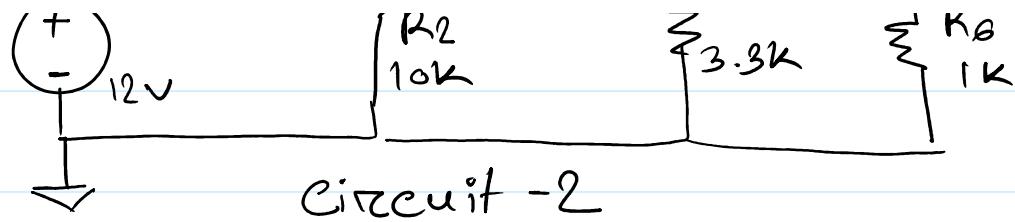

(6)

Showing all the steps, theoretically calculate R_{eq} of circuit 1.
 Compare with the experimental value.




Table 2:

Experimental readings				Theoretical values			
I_s	I_{R1}	I_{R2}	I_{R3}	I_s	I_{R1}	I_{R2}	I_{R3}
4.098 mA	1.788 mA	1.856 mA	1.059 mA				
% Error							
I_s	I_{R1}		I_{R2}		I_{R3}		


We gather the data from multimeter using a multimeter and setting it to reading mode to Amp.

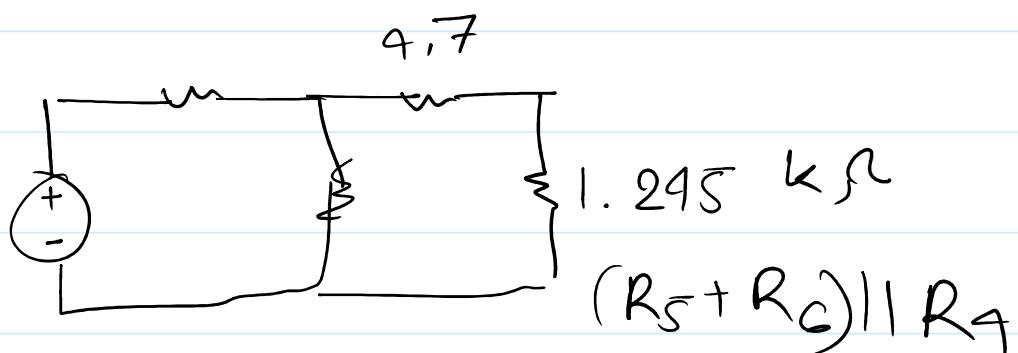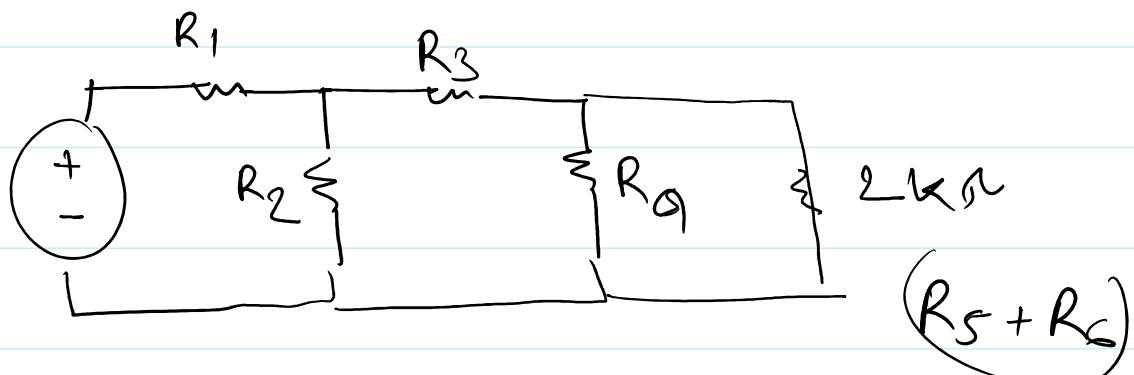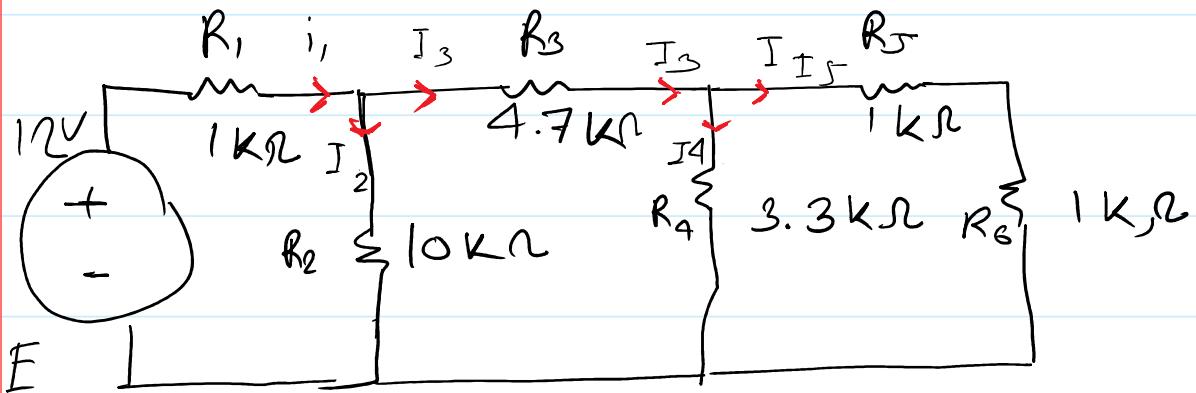(7)


Calculate all the theoretical values for Table 5. Show all steps




$\alpha_{in} = 1.7$

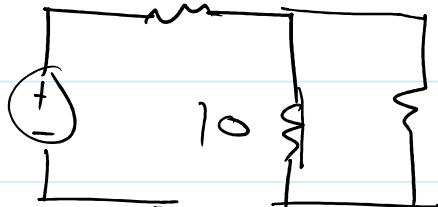

$$5.945 \text{ k}\Omega \quad ((R_5 + R_6) || R_9) + R_3$$

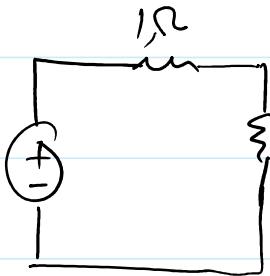

$$3.728 \text{ }\Omega \quad ((R_5 + R_6) || R_9) + R_3 \parallel R_2$$

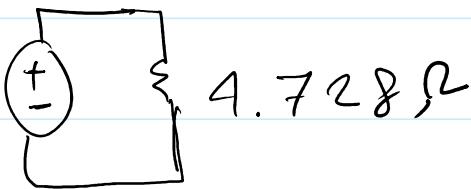

$$R_{eq} = 4.728 \text{ k}\Omega$$

$$I_1 = I_2 + I_3$$

$$I_3 = I_4 + I_5$$

we get

$$I_1 = I_2 + I_4 + I_5$$

$$V_1 = \frac{R_1}{R_{eq}} \times 12 = 2.538 \text{ V}$$

$$I_1 = \frac{V_1}{R_1} = \frac{2.538}{1} = 2.538 \text{ A}$$

$$V_2 = E - V_1 \quad [\text{voltage rule}]$$

$$\approx 12 - 2.538 \approx 9.46 \text{ V}$$

$$I_2 = \frac{V_2}{R_2} = \frac{9.46}{10} = 0.946 \text{ A}$$

$$V_3 = \frac{R_3}{((R_S + R_C) \parallel R_A) + R_3} \times V_2$$

$$= \frac{4.7}{((1+1)^{-1} + 3.3^{-1})^{-1} + 4.7} \times 9.46$$

$$\approx 7.478 \text{ V}$$

$$I_3 = \frac{V_3}{R_3} = \frac{7.478}{4.7} = 1.592 \text{ A}$$

$$V_A = 9.46 - 7.478 = 1.982 \text{ V} \quad [\text{voltage rule}]$$

$$I_A = \frac{V_A}{R_A} = \frac{1.982}{3.3} = 0.601 \text{ A}$$

$$V_5 = \frac{R_S}{R_S + R_6} \times V_4$$

$$= \frac{1}{1+1} \times 1.982$$

$$= 0.991$$

$$I_5 = \frac{V_5}{R_S} = \frac{0.991}{1} = 0.991 \text{ A}$$

$$V_6 = V_5 - V_4 = 1.982 - 0.991 = 0.991 \text{ V}$$

$$I_6 = \frac{R_6}{R_S + R_6} \times V_4$$

$$I_6 = \frac{1}{1+1} \times 1.982 = 0.991 \text{ A}$$

Table 5:

Component	Voltage	Current mA
E	12	2.538
R1	2.53	2.538
R2	3.96	0.946
R3	7.48	1.592
R4	1.58	0.601
R5	0.99	0.991
R6	0.99	0.991

Discussion:

From this lab-2 we can have learn how current division rule works. Also how Kirchhoff's voltage law work, checked its validity with hands on experiment. Stated proof from experimental data, and how get voltage and current rating from diagram.

As, it was an online lab, we had to

we managed to do the experiments.
So, we didn't have to face many errors

Theory:-

Formulas.

If, we had done the labs offline then we could have faced errors like human errors, loose wiring errors, environmental errors, mechanical errors. Also can faces errors using DMM, cables and breadboard etc. Because of Online we are