

Bushra Hossain - 2031346642, Md. Ishtiaq Ahamed
Fahim - 2012518642, Tajrian Al Israq - 2021536643
LAB-4

Saturday, 12 March 2022 10:48 PM

Spring 2022
EEE/ETE 141L
Electrical Circuits-I Lab(Sec-10)
Faculty : Md. Abu Obaidah (AbO)
Instructor: Farhana Atuyar Saleh

Lab No.: 04

Date of Performance : 09/03/2022

Name:

1. **Bushra Hossain**
2. **Md. Ishtiaq Ahamed Fahim**
3. **Tajrian Al Israq**

Date of Submission : 16/03/2022

ID:

1. **2031346642**
2. **2012518642**
3. **2021536643**

Lab 4: Delta-Wye Conversion


Objectives:

- ① We have to perform Delta-Wye Conversion.
- ② We have to verify the results with measured data.
- ③ We have to solve a complex circuit using Delta-Wye Conversion.


List of Equipment:

- ① Trainer Board
- ② DMM
- ③ $5 \times 15\ \Omega$ resistor
- ④ $3 \times 5\ \Omega$ resistor
- ⑤ Multisim.

~~Def~~ Circuit Diagram :

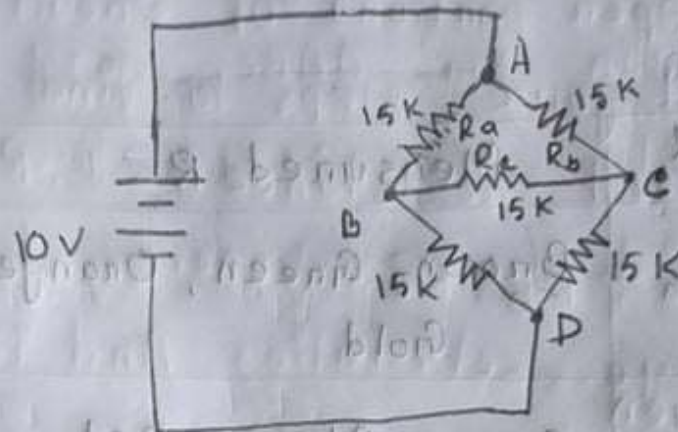

Circuit - 1

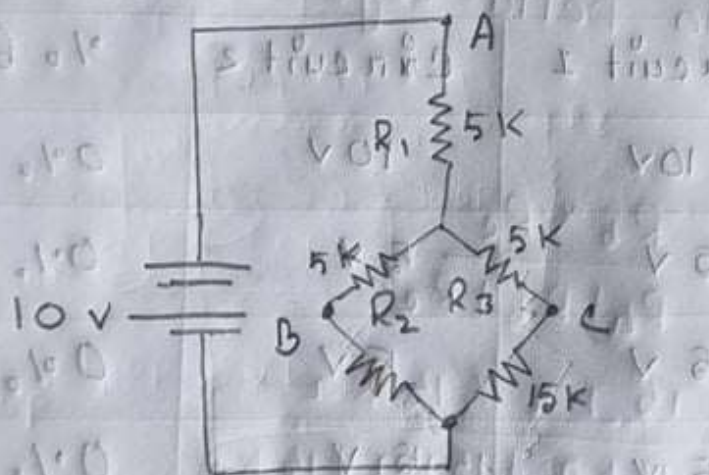

Circuit - 2

Data Table :

Table 1 :

Theoretical R	Measured R	% Error
15 K	Brown, Green, Orange, Gold	0%
5 K	Green, Black, Red, Gold	0%

Table 2 :

Readings	Circuit 1	Circuit 2	% Error
V_{AD}	10V	10V	0%
V_{BD}	5V	5V	0%
V_{CD}	5V	5V	0%
V_{AB}	5V	5V	0%
V_{BC}	0V	0V	0%
V_{AC}	5V	5V	0%

Question / Answer :

① The resistors in circuit-1 are in series or in parallel combination?

Ans: The resistors in circuit-1 are neither in series nor in parallel combination.

The resistors are in a complex combination.

② What techniques would you use to find the equivalent resistance?

Ans: I would use Delta-Wye conversion techniques to find the equivalent resistance.

$$R_s = \frac{R_1 \times R_2}{R_1 + R_2 + R_3}$$

③ Perform Delta-wye conversion for ΔABC (upper portion) of circuit 1.

Show all your steps to find the equivalent resistance R_1, R_2, R_3

from R_a, R_b, R_c .

Ans: Given,

$$R_a = 15 \text{ k}\Omega, R_b = 15 \text{ k}\Omega, R_c = 15 \text{ k}\Omega$$

According to Delta-wye conversion

formula,

$$R_1 = \frac{R_b \times R_c}{R_a + R_b + R_c}$$

$$= \frac{15 \text{ k}\Omega \times 15 \text{ k}\Omega}{15 \text{ k}\Omega + 15 \text{ k}\Omega + 15 \text{ k}\Omega}$$

$$= 5 \text{ k}\Omega$$

$$R_2 = \frac{R_a \times R_c}{R_a + R_b + R_c}$$

$$= \left(\frac{15 \times 15}{15 + 15 + 15} \right) \text{ k}\Omega$$


of wattage $= 15 \text{ K}\Omega$ after two nodes

$$R_3 = \frac{R_a \times R_b}{R_a + R_b + R_c}$$

$$= \frac{15 \text{ K}\Omega \times 15 \text{ K}\Omega}{15 \text{ K}\Omega + 15 \text{ K}\Omega + 15 \text{ K}\Omega}$$

$$= 5 \text{ K}\Omega$$

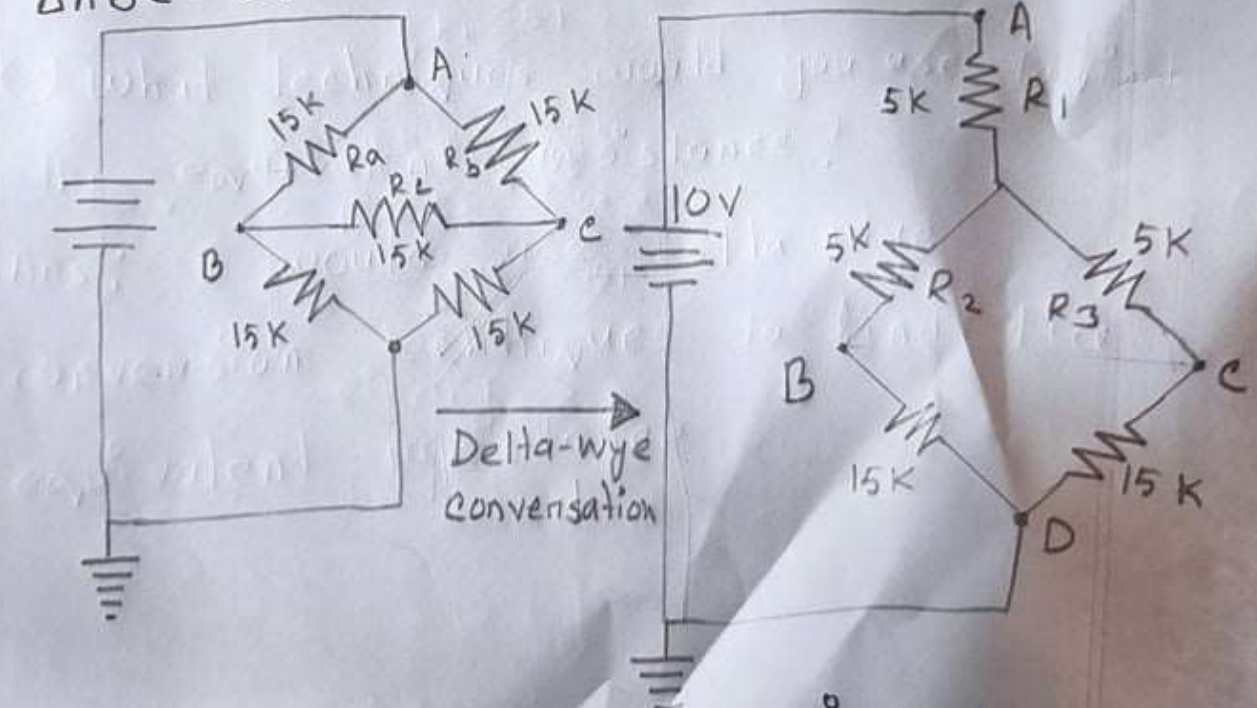④ Redraw the equivalent circuit after applying the Delta-Wye conversion for ΔABC . Is it same as circuit-2?







After Redrawing the equivalent




circuit after applying the Delta-Wye conversion for ΔABC everything is exactly same except the values of individual resistances of the Delta-Wye schematics. And it is same as circuit-2.

5. Calculate Req.



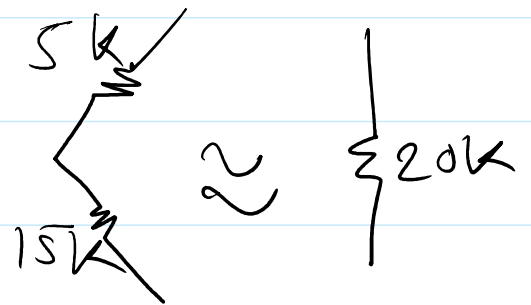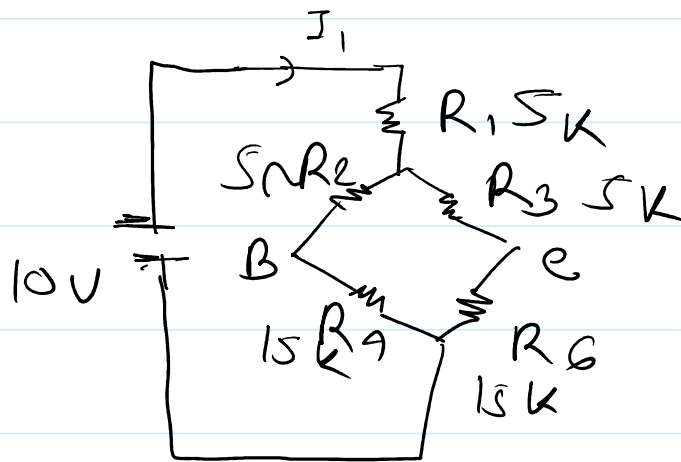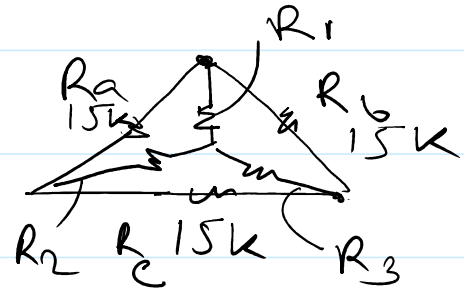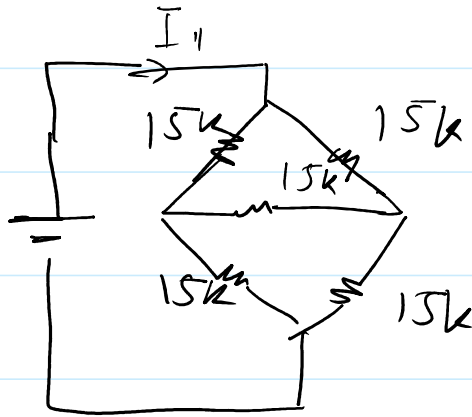

$$R_s = 5 + 15 = 20k$$

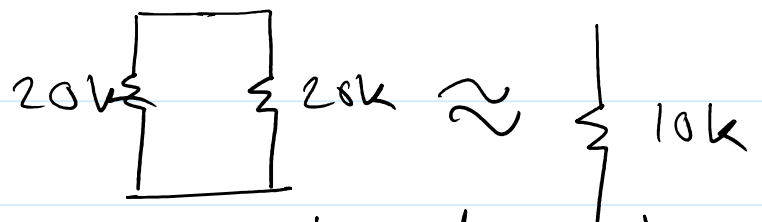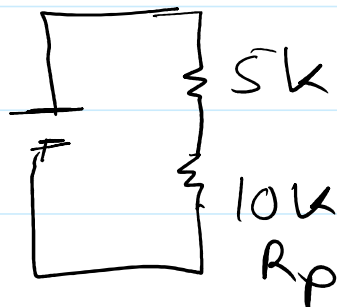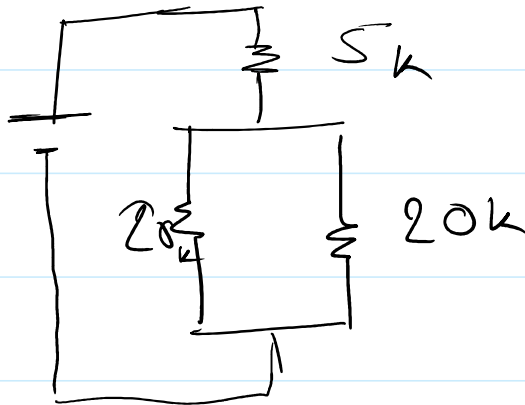


$$\frac{1}{R_p} = \frac{1}{R_s} + \frac{1}{R_s}$$

$$\begin{aligned}
 R_{eq} &= R_1 + R_p \\
 &= (5 + 10) \text{ k} \\
 &= 15 \text{ k} \quad (\text{Ans})
 \end{aligned}$$

$$\begin{aligned}
 \frac{1}{R_p} &= \frac{1}{20} + \frac{1}{20} \\
 \frac{1}{R_p} &= \frac{2}{20} \\
 R_p &= 10 \text{ k}
 \end{aligned}$$

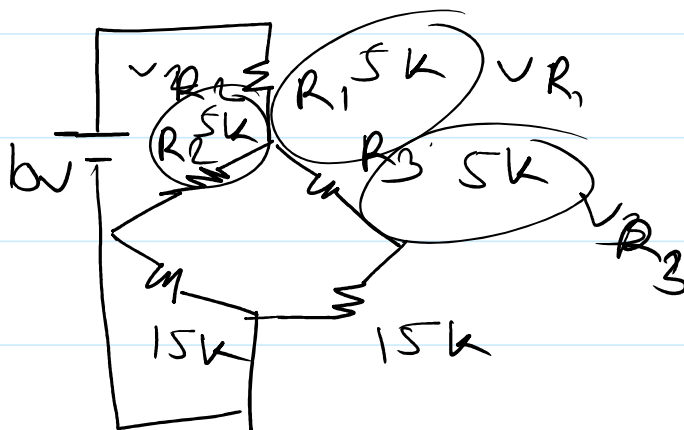6. Calculate the voltage of R_1, R_2, R_3



$$R_{eq} = 15 \text{ k}$$

$$E = 10 \text{ V}$$

$$I_1 = \frac{E}{R} = \frac{10}{15} = \frac{2}{3} = 0.67 \text{ A}$$

$$V_{R_1} = I_1 R_1 = 0.67 \times 5 = 3.35 \text{ V}$$


$$V_{R_2} = (10 - 3.35) \frac{R_2}{R_2 + 15}$$


$$= 6.65 \times \frac{5}{5 + 15} = 1.675 \text{ V}$$

$$V_{R_3} = (10 - 3.35) \frac{R_3}{R_3 + 15}$$

$$= 6.65 \times \frac{5}{5 + 15} = 1.675 \text{ V}$$

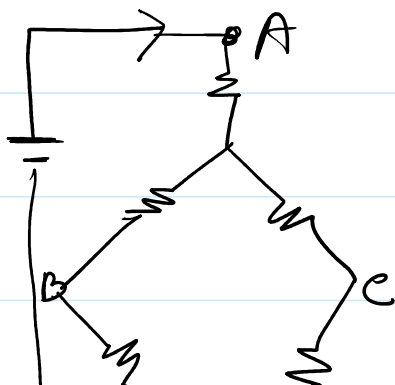7. Calculate V_{AB} , V_{BC} , V_{AC} and V_{AD} , V_{BD} , V_{CD} . Do your calculated values match the measured values for circuit 2? Find the % Error



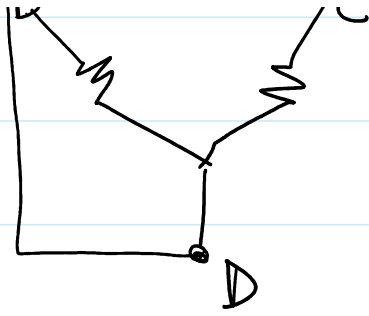

$$V_{AB} = V_{R_1} + V_{R_2} = 1.67 \text{ V} + 3.33 \text{ V} \\ = 5.00 \text{ V}$$

$$V_{BC} = V_{R_2} - V_{R_3} \quad [\text{using KVL}] \\ = (1.67 - 1.67) \quad \left[\begin{array}{c} + \\ - \end{array} \right] \\ = 0 \text{ V}$$

$$V_{AC} = V_{R_1} + V_{R_3} \\ = (1.67 - 3.33) \text{ V}$$

$$V_D = E - V_{R_1} - V_{R_2} \\ = 10 - 3.3 - 1.67 \\ = 10 - 5 \\ = 5 \text{ V}$$

$$\begin{aligned}
 V_{AD} &= V_{AB} + V_{BC} + V_{RBD} \\
 &= (3.33 + 1.67 + 5)V \\
 &= 10V
 \end{aligned}$$

$$\begin{aligned}
 V_{CD} &= E - V_{R1} - V_{R3} \\
 &= 10 - 3.3 - 1.67 \\
 &= 10 - 5 \\
 &= 5V
 \end{aligned}$$

we know

$$\% \text{ Error} = \frac{\text{Theoretical} - \text{Experimental}}{\text{Theoretical}} \times 100\%$$

Circuit - 2

Reading	Theoretical	Experimental	% Error
V_{AB}	5V	5V	$\frac{5-5}{5} \times 100\% = 0\%$
V_{BC}	0V	0V	$\frac{0-0}{0} \times 100\% = 0\%$
V_{AC}	5V	5V	$\frac{5-5}{5} \times 100\% = 0\%$
V_{AD}	10V	10V	$\frac{10-10}{10} \times 100\% = 0\%$
V_{BD}	5V	5V	$\frac{5-5}{5} \times 100\% = 0\%$
V_{CD}	5V	5V	$\frac{5-5}{5} \times 100\% = 0\%$

8. Using Table 2, analyze whether Circuit 2 is equivalent to Circuit 1? Was Delta-Wye conversion successful?

table -2

Reading	circuit-1	circuit-2	% Error	was Delta-Wye successful?
V_{AD}	10 V	10 V	0%	Yes, extremely Accurate
V_{BD}	5V	5V	0%	Yes, extremely Accurate
V_{CD}	5V	5V	0%	Yes, extremely Accurate
V_{AB}	5V	5V	0%	Yes, Extremely Accurate
V_{BC}	0V	0V	0%	Yes, Extremely Accurate
V_{AC}	5V	5V	0%	Yes, Extremely Accurate

As wye Delta conversion yielded the same circuit as circuit 2.

And since circuit 1 and 2 are totally equivalent we can say for more wye delta was successful.

Discussion :

From this lab we can learn wye Delta convention that helps us solve for circuit which can not be said series or parallel and to calculate its equivalent value circuit and to calculate it.

As in a lab on multimeter software there is no error that might have been arisen.

Both multimeter and load effect has the same result. As in a software Based lab we don't have flaws that might have arisen from accuracy problem loose connection human error, or on DMM, cables,

breadboard connection etc.